




Chandigarh

Mid Term Examination(18192)

Programme: B.Tech (ECE)  
Course Name: Digital Design  
Maximum Marks:25

Year/Semester: 1st/2<sup>nd</sup>  
Course Code: ECN 103  
Time allowed:1:30 Hours

 - 1) How many bits would be required to encode decimal numbers from 0 to 9999 in straight binary and BCD codes. What would be the BCD equivalent of decimal number 27 in 16 bit representation. 2
- 2) Using Q M (Quine McCluskey) method find the minimum SOP for  $f(A,B,C,D)=\Sigma(1,2,3,9,12,13,14) + d(0,7,10,15)$ .  
Implement the simplified expression using following two level implementations:  
(i) AND NOR (ii) NAND AND (iii) OR NAND (iv) NOR OR 10
- 3) What are parity generator and parity checker circuits? Explain an odd parity generator and checker circuit for a 3 bit data input using truth table and logical implementation. Only two input XOR and XNOR gates are available. 6
- 4) Implement the function  $F(A,B,C)=\Pi(1,2,5)$  using (i) 4:1 Mux (ii) Suitable Decoder 4
- 5) IC 7483 is a 4 bit adder. Show how can you build 8 bit adder subtractor using IC 7483.Pin configuration of IC 7483 is as under:






EXPLORE INNOVATE EXCEL

**Punjab Engineering College (Deemed to be University)****Chandigarh****End-Term Examination(18192)**Programme: **B.Tech (ECE)**Course Name: **Digital Design**Maximum Marks: **80**Year/Semester: **1st/2<sup>nd</sup>**Course Code: **ECN 103**Time allowed: **3 Hours****Notes**

- All questions are compulsory.
- Unless stated otherwise, the symbols have their usual meanings in context with subject. Assume suitably and state, additional data required, if any.
- The candidates, before starting to write the solutions, should please check the question paper for any discrepancy, and also ensure that they have been delivered the question paper of right course code

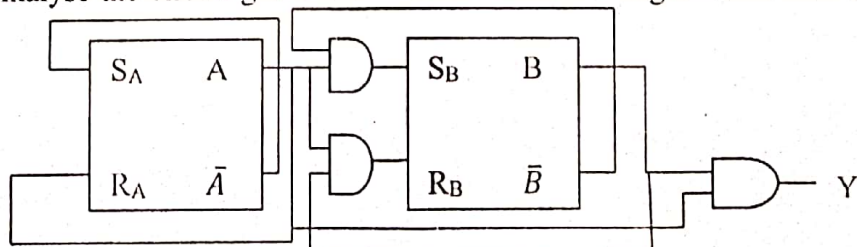Q. No.		Marks
1.	<p>a) Implement (i) a three input Ex-NOR function using only two input Ex NOR gates(ii) a three input NAND gate using two input NAND gates.</p> <p>b) Prove that <math>\bar{L}(M + \bar{N}) + \bar{L}\bar{P}Q = (L + \bar{P}Q)(\bar{L} + M + \bar{N})</math> using Boolean rules and laws.</p> <p>c) List the eight degenerate two level forms and show that they reduce to a single operation.</p>	<p>4</p> <p>2</p> <p>4</p>
2	<p>a) Given the Boolean function <math>Y(A,B,C,D)=\prod M(1,2,3,8,9,10,11,14)+d(7,15)</math>. Simplify using K maps and obtain the answer in Product of Sums form. <math>\bar{A}B + CD</math> is a simplified expression of the expression</p> <p>b) <math>ABCD + \bar{A}\bar{B}CD + \bar{A}B</math>. Determine if there are any don't cares.</p>	<p>6</p> <p>4</p>
3.	<p>a) Show that how 2 two bit numbers can be compared using (i) 16:1 MUX (ii) 8:1 MUX (iii) Suitable Decoder.</p> <p>b) Show the implementation of a four bit adder subtractor using full adders and with a provision of detecting overflow. Explain the operation of circuit for signed as well as unsigned numbers.</p>	<p>6</p> <p>4</p>
4.	<p>a) Derive the characteristic equation of RS flip flop. Give excitation table of RS flip flop. Analyse the circuit given below. Draw the state diagram and state analysis table.</p> 	7



	b)	Convert JK flip flop to D flip flop.	3														
5	a)	Show and explain the logic arrangement for a parallel in parallel out shift register. Also show the wiring arrangement to effect a shift left operation.	4														
	b)	The IC 74LS174 datasheet gives a set up time of 20 ns and a hold Time of 5 ns .What is the minimum required width of data input levels for 74LS174.Also define set up time and hold time.	3														
	c)	What is a decade counter? Design Mod 5 counter and then build decade counter by cascading mod 5 and mod 2 counter. From the cascaded circuit, draw the output waveforms and write the count sequence obtained..	5														
	d)	Draw the block diagram of Mealy and Moore Finite State Machines. Compare the two	3														
6.	a)	Draw a PLA circuit to implement the function by making the PLA programming table $F_1 = \bar{A}B + A\bar{C} + \bar{A}B\bar{C}$ $F_2 = \overline{(AC + AB + BC)}$	6														
	b)	Define propagation delay, power dissipation , fanout and Noise Margin Parameter logic family.	6														
	c)	How many inputs of a low power Schottky TTL NAND gate can be reliably driven from a single output of Schottky TTL NAND gate given the following parameters. <table border="1"><thead><tr><th></th><th><math>I_{OH}</math></th><th><math>I_{OL}</math></th><th><math>I_{IH}</math></th><th><math>I_{IL}</math></th></tr></thead><tbody><tr><td>Schottky TTL</td><td>1 mA</td><td>20 mA</td><td>0.05 mA</td><td>2 mA</td></tr><tr><td>Low Power Schottky TTL</td><td>0.4 mA</td><td>8 mA</td><td>0.02 mA</td><td>0.4 mA</td></tr></tbody></table>		$I_{OH}$	$I_{OL}$	$I_{IH}$	$I_{IL}$	Schottky TTL	1 mA	20 mA	0.05 mA	2 mA	Low Power Schottky TTL	0.4 mA	8 mA	0.02 mA	0.4 mA
	$I_{OH}$	$I_{OL}$	$I_{IH}$	$I_{IL}$													
Schottky TTL	1 mA	20 mA	0.05 mA	2 mA													
Low Power Schottky TTL	0.4 mA	8 mA	0.02 mA	0.4 mA													
7	a)	Explain parallel comparator type A/D converter for a 3 bit digital Output.	6														
	b)	What are the output voltages caused by each bit in 5 bit ladder if input levels are 0 = 0V and 1= 10 V. Calculate the output that has a digital input 11010.Can output reach 10V.If yes, for what digital input combination.	4														